

**ΑΠΟΛΥΤΗΡΙΕΣ ΕΞΕΤΑΣΕΙΣ ΤΗΣ Γ' ΛΥΚΕΙΟΥ
ΗΛΕΚΤΡΟΛΟΓΙΑ ΤΕΧΝΟΛΟΓΙΚΗΣ ΚΑΤΕΥΘΥΝΣΗΣ**

ΟΙ ΑΠΑΝΤΗΣΕΙΣ ΤΩΝ ΘΕΜΑΤΩΝ ΑΠΟ ΚΑΘΗΓΗΤΕΣ
ΤΟΥ ΦΡΟΝΤΙΣΤΗΡΙΟΥ



www.orion.edu.gr

ΟΜΑΔΑ ΠΡΩΤΗ

A1.1. δ, **A1.2.** α, **A1.3.** β, **A1.4.** α

A2. $(9A)_{16} = 9 \cdot 16^1 + 10 \cdot 16^0 = 154 = 1 \cdot 10^2 + 5 \cdot 10^1 + 4 \cdot 10^0 = (154)_{10}$

$$154 = 128 + 16 + 8 + 2 = 1 \cdot 2^7 + 0 \cdot 2^6 + 0 \cdot 2^5 + 1 \cdot 2^4 + 1 \cdot 2^3 + 0 \cdot 2^2 + 1 \cdot 2^1 + 0 \cdot 2^0 =$$
$$= (10011010)_2$$

A3.

$$\begin{pmatrix} x & y & z & f \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 1 \\ 1 & 0 & 0 & 0 \\ 1 & 0 & 1 & 1 \\ 1 & 1 & 0 & 1 \\ 1 & 1 & 1 & 1 \end{pmatrix}$$

A4. Έχουμε παράλληλη σύνδεση:

$$\frac{1}{R_{AB}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{3}{R} \Rightarrow R_{AB} = \frac{R}{3} = \frac{12\Omega}{3} = 4 \Omega$$

A5. α. Από το σχολικό βιβλίο, σελ. 169:

«Ο λόγος των V_{CE} σταθερή»

$$\beta. \quad \beta = \frac{\Delta I_C}{\Delta I_B} = \frac{5\text{mA}}{100\mu\text{A}} = \frac{5 \cdot 10^{-3} \text{A}}{100 \cdot 10^{-6} \text{A}} = 50 \quad (\text{πάνω καμπύλη})$$


και όμοια στις άλλες.

ΟΜΑΔΑ ΔΕΥΤΕΡΗ

$$\mathbf{B1. \alpha.} \quad V_{AB} = IR_1 = \frac{R_1}{R_1 + R_2} V = \frac{6}{6+3} \cdot 72\text{V} = 48\text{V}$$

$$V_{BF} = IR_2 = \frac{R_2}{R_1 + R_2} V = \frac{6}{6+3} \cdot 72\text{V} = 24\text{V}$$
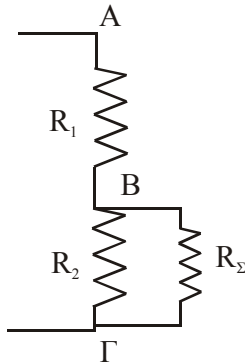
$$\beta. \quad P_K = \frac{V_K^2}{R_\Sigma} \Rightarrow R_\Sigma = \frac{V_K^2}{P_K} = \frac{24^2}{96} \Omega = 6 \Omega \quad \text{συσκευής}$$



$$R_{\text{ολ}} = R_1 + \frac{R_2 \cdot R_\Sigma}{R_2 + R_\Sigma} = \left(6 + \frac{3 \cdot 6}{3+6} \right) \Omega = 8 \Omega$$

$$I_{\text{ολ}} = \frac{V}{R_{\text{ολ}}} = \frac{72}{8} \text{A} = 9 \text{A}$$

$$R_{2\Sigma} = \frac{R_2 \cdot R_\Sigma}{R_2 + R_\Sigma} = \frac{3 \cdot 6}{3+6} \Omega = 2 \Omega$$

Άρα $V_\Sigma = V_{BF} = I_{\text{ολ}} R_{2\Sigma} \Rightarrow V_\Sigma = 9 \cdot 2\text{V} = 18\text{V} \neq V_K$ και η συσκευή δεν λειτουργεί κανονικά.

$$\gamma. \quad V_{BF} = V_K = 24\text{V} \quad , \quad R_{2\Sigma} = 2 \Omega \quad , \quad I'_{\text{ολ}} = \frac{V_{BF}}{R_{2\Sigma}} = \frac{24}{2} \text{A} = 12\text{A}$$

$$V_{AB} = V - V_{BF} = (72 - 24)\text{V} = 48\text{V}$$

$$V_{AB} = I'_{\text{ολ}} \cdot R_3 \Rightarrow R_3 = \frac{V_{AB}}{I'_{\text{ολ}}} = \frac{48}{12} \Omega = 4\Omega$$

B2. α. $A_I = \frac{I_{0,\epsilon\xi}}{I_{0,\epsilon\sigma}} \Rightarrow I_{0,\epsilon\xi} = A_I \cdot I_{0,\epsilon\sigma} = 10^3 \cdot 0,5\text{mA} = 0,5\text{A}$

$$\text{dB}_{\epsilon\text{VT}} = 20 \log A_I = 20 \cdot \log 10^3 = 60$$

β. $\text{dB}_{\text{τασ.}} = 20 \log \frac{V_{0,\epsilon\xi}}{V_{0,\epsilon\sigma}} \Rightarrow 80 = 20 \log \frac{V_{0,\epsilon\xi}}{V_{0,\epsilon\sigma}} \Rightarrow$

$$\Rightarrow \log \frac{V_{0,\epsilon\xi}}{V_{0,\epsilon\sigma}} = 4 \Rightarrow \frac{V_{0,\epsilon\xi}}{V_{0,\epsilon\sigma}} = 10^4 = A_V$$

και $A_P = A_I \cdot A_V = 10^3 \cdot 10^4 = 10^7 = \frac{P_{\epsilon\xi}}{P_{\epsilon\sigma}}$, οπότε:

$$\text{dB}_{\text{ισχ.}} = 10 \log \frac{P_{\epsilon\xi}}{P_{\epsilon\sigma}} = 10 \cdot \log 10^7 = 70$$

B3. Με $i = 4\eta\mu 500t$ ή $i = I_0\eta\mu\omega t$ έχουμε: $I_0 = 4\text{A}$, $\omega = 500\text{rad/s}$

α. $x_c = \frac{1}{\omega c} = \frac{1}{500 \cdot 100 \cdot 10^{-6}} \Omega = 20 \Omega$

β. $Z = \sqrt{R^2 + x_c^2} = \sqrt{20^2 + 20^2} \Omega = 20\sqrt{2}\Omega$

γ. $V_0 = I_0 \cdot Z = 4 \cdot 20\sqrt{2}\text{V} = 80\sqrt{2}\text{V}$

$$V_{0C} = I_0 X_C = 4 \cdot 20\text{V} = 80\text{V}$$

$$V_C = V_{0C} \eta\mu \left(\omega t - \frac{\pi}{2} \right) = 80 \eta\mu \left(500t - \frac{\pi}{2} \right),$$

$$V = V_0 \eta\mu(\omega t - \varphi), \quad \cos\varphi = \frac{R}{Z} = \frac{20}{20\sqrt{2}} = \frac{\sqrt{2}}{2} \Rightarrow \varphi = \frac{\pi}{4}$$

οπότε: $V = 80\sqrt{2}\eta\mu \left(500t - \frac{\pi}{4} \right)$

$$\delta. \quad P_{\text{πραγμα}} = \frac{1}{2} V_0 I_0 \cos \varphi = \frac{1}{2} 80\sqrt{2} \cdot 4 \cdot \frac{\sqrt{2}}{2} \text{ W} = 160 \text{ W}$$

$$Q_{\text{αεργ.}} = \frac{1}{2} V_0 I_0 \eta \mu \varphi = \frac{1}{2} 80\sqrt{2} \cdot 4 \cdot \frac{\sqrt{2}}{2} \text{ W} = 160 \text{ W}$$

$$S_{\varphi_{\text{αιν.}}} = \frac{1}{2} V_0 I_0 = \frac{1}{2} 80\sqrt{2} \cdot 4 \text{ W} = 160\sqrt{2} \text{ W}$$

$$\epsilon. \quad x_C = x_L \Rightarrow \frac{1}{C\omega} = L\omega \Rightarrow L = \frac{1}{C\omega^2} \Rightarrow L = \frac{1}{100 \cdot 10^{-6} \cdot 500^2} \text{ H} = \frac{1}{25} \text{ H}$$